



## Avinashilingam Institute for Home Science and Higher Education for Women

(Deemed to be University under Category 'A' by MHRD, Estd. u/s 3 of UGC Act 1956)

Re-accredited with 'A+' Grade by NAAC. Recognised by UGC Under Section 12B

Coimbatore - 641 043, Tamil Nadu, India

### Bachelor's Degree Examination – June 2021 VI Semester

**Class : III UG**  
**Major : Physics**

**Time : 3 Hours**  
**Max. Marks: 100**

#### 18BPHC21 Digital Electronics

##### Part A

10 X 1 =10

##### Choose the Correct Answer

1. The number system, Which uses alphabets as well as numerals is CO1 K1  
a. Binary                      b. Octal                      c. Decimal                      d. Hexadecimal
2. A person represents himself as being  $(01011)_2$  year old. What is his actual age? CO1 K3  
a. 11                      b. 35                      c. 15                      d. None of the above
3. The logic expression  $AB+AB$  can be implemented by given input and B to a two input CO2 K2  
a. NORgate                      b. Exclusive NOR gate                      c. Exclusive OR gate                      d. NAND
4. Which of the following is known as half adder CO2 K1  
a. XOR gate                      b. XNOR gate                      c. NAND gate                      d. NOR gate
5. A decimal number 6 in excess -3 code is written as CO3 K2  
a. 0110                      b. 0011                      c. 1101                      d.1001
6. The total number of cell in the Karnaugh map of a switching function (A, B, C) consist of only three variables are CO3 K2  
a. 4                      b. 8                      c. 16                      d. 3
7. Which of the flip flop is used to eliminate race around problem CO4 K2  
a. Master slave J- K flip flop                      b. R-S flip flop  
c. J-K flip flop                      d. D flip flop
8. How many flip-flops are required to construct a mod-64 ripple counter? CO4 K3  
a. 32                      b. 8                      c. 6                      d. None of the all
9. The contents of memory into blocks of the same size is called as CO5 K2  
a. ROM                      b. EPROM                      c. EEPROM                      d. All the above
10. Which one of the following has capability to store data in extremely high densities? CO5 K1  
a. Register                      b. Semiconductor                      c. Capacitor                      d. flip flop

**Part B**  
**Answer ALL questions**  
**Each answer should not exceed 400 words or two pages**

**5 X6 = 30**

11. a. Simplify the following binary operation. CO1K4  
 i..1011.01+1001.11      ii. 110.01-100.1      iii.101.01\*11  
 (or)
- 11.b. Convert following decimal number into an equivalent binary numbers CO1 K4  
 i.. 41      ii. 1996
12. a. Draw OR, AND and NAND gates using diodes. CO2 K3  
 (or)
- 12.b State and Prove the De Morgan's theorems. CO2 K4
13. a. Calculate the value of resistor for 2ma current through LED and 5V  
 power supply with forward voltage drop of 2V. CO3 K3  
 (or)
- 13.b. Explain Gray code in terms of Binary to Gray and Gray to Binary converter. CO3 K3
- 14.a. Discuss about pulse triggering JK flip-flop. CO4 K3  
 (or)
- 14.b. Design mod 5 ripplecounter using D flip-flop and the wave form. CO4K4
- 15.a. Explain aboutRead Only Memory (ROM) . CO5 K3  
 (or)
- 15.b. Discuss Programmable Read only Memory (PROM). CO5 K3

**Part C**  
**Answer ALL questions**  
**Each answer should not exceed 800 words or four pages**

**5X 12 = 60**

- 16.a. What is BCD code and convert 63718decimal into equivalent CO1 K6  
 i. Binary ii. Octal iii. Hexadecimal  
 (or)
- 16.b. Define 1's and 2's complements and Perform the following subtraction using 1's and 2's  
 complements CO1 K6  
 i. 10111.0-10011.1,  
 ii. 11011 – 11001
- 17.a. Discuss NOR gate in detail and show how it can be used as universal gate CO2 K4  
 (or)
- 17.b. Design Full Subtractor using NAND gates and explainits operation. CO2 K4
- 18.a. Obtain the minimal POS expression for the switching function given below using CO3 K6  
 4-variable Karnaugh map  $f(A, B, C, D)= \Sigma(0, 1, 2, 3, 4, 7, 8, 11, 12, 13, 14, 15)$   
 (or)
- 18.b. Explain Error detection and correction method using parity method. CO3 K5
- 19.a. Design and explain about 8-bit up-down Synchronous counter. CO4 K4  
 (or)
- 19.b. Construct and explain Serial-In Serial-out and Parallel-In -Serialout shift registers and CO4 K4  
 write two of its applications each
- 20.a. Describe the Random access memory (RAM) and summarize the operation of CO5 K3  
 7489 chip and explain how it can be used in gadget  
 (or)
- 20.b. Discuss Electrically Programmable Read only Memory(EPROM) with logic CO5 K3  
 diagram and its advantages.

\*\*\*\*\*