



**Part B**

**5 x6 =30**

**Answer ALL questions**

**Each answer should not exceed 400 words or two pages**

- 11.a. Explain the Binary Code system with appropriate examples. CO1K2  
(or)  
11.b. Explain Error Detecting and Correcting Codes briefly. CO2K1
- 12.a. What are the laws and rules of Boolean algebra? List and explain them. CO2K1  
(or)  
12.b. What is a Half Adder? Explain its functionality with a diagram and truth table CO2K2
- 13.a. Write a comprehensive short note on Multiplexer and Demultiplexer, highlighting their uses and working principles. CO3K4  
(or)  
13.b. Explain Programmable Logic Array and its characteristics in detail. CO3K4
- 14.a. How does an RS Flip-Flop work? Explain with a detailed analysis and truth table. CO4K3  
(or)  
14.b. What are the applications of Shift Registers? Explain in detail. CO4K4
- 15.a. Describe the working of a Ring Counter and its significance in digital circuits. CO5K2  
(or)  
15.b. Describe Memory Addressing with examples. CO5K2

**Part C**

**5 x 12 =60**

**Answer ALL questions**

**Each answer should not exceed 800 words or four pages**

- 16.a. Explain the following conversions with examples:  
i. Decimal to Binary conversion    ii. Decimal to Octal conversion CO1K1  
(or)  
16.b. Give a detailed summary of Logic Gates along with their truth tables and functions.. CO1K2
- 17.a. How can Boolean expressions be simplified using the Karnaugh Map (K-Map) method? Explain with a truth table and examples. CO2K1  
(or)  
17.b. Explain the different types of Universal Gates with their truth tables. CO2K2
- 18.a. Explain Encoders and Decoders in detail with a diagram. CO3K2  
(or)  
18.b. What are the uses of a Parity Generator and Parity Checker? Explain their working principles with the help of a diagram. CO3K4
- 19.a. Explain in detail the following topics:  
i. Master-Slave Flip-Flops  
ii. JK Flip-Flops, including their working principles and applications. CO4K2  
(or)  
19.b. Provide a detailed explanation of the different types of Shift Registers with examples. CO4K2
- 20.a. Explain the concepts of Up-Down counters and Synchronous counters. CO5K2  
(or)  
20.b. Explain the various types of RAM and ROM, highlighting their characteristics and uses. CO5K2

\*\*\*\*\*