

Part B
Answer the following
Answer should not exceed 400 words or two pages

5 X 6=30

- 11.a. Write short notes on code conversion.
(or)
11.b. Draw NAND and NOR gates with truth tables.
- 12.a. Discuss about K-map.
(or)
12.b. Prove De Morgan's theorem 1 and 2.
- 13.a. Draw 2-to-4 decoder and explain its function.
(or)
13.b. Explain multiplexer with circuit.
- 14.a. Define flip flops and its uses.
(or)
14.b. Draw D flip flop diagram and explain.
- 15.a. Sketch the types of ROM and its functions.
(or)
15.b. List the memory addressing and its uses.

Part C
Answer the following
Answer should not exceed 800 words or four pages

5 x 12=60

- 16.a. Interpret $(ABCD)_{16}$, $(F011)_{16}$ and $(FFFF)_{16}$ into binary.
(or)
16.b. Review the logic gates and tabulate their truth values.
- 17.a. Describe Boolean Laws.
(or)
17.b. Sketch the half-adder and full-adder with relevant information.
- 18.a. Apply encoder concept for 8-to-3 lines and write detail.
(or)
18.b. Illustrate demultiplexers with neat diagram.
- 19.a. Compare R-S, J-K and D flip flops.
(or)
19.b. Inspect the types of shift registers with TT.
- 20.a. Analyze the Asynchronous counters.
(or)
20.b. Demonstrate the synchronous counters.
